

# Boost Converter Analysis | ED18B027


⋮ Tag Empty

▼ Status Empty

✓ 1 more property
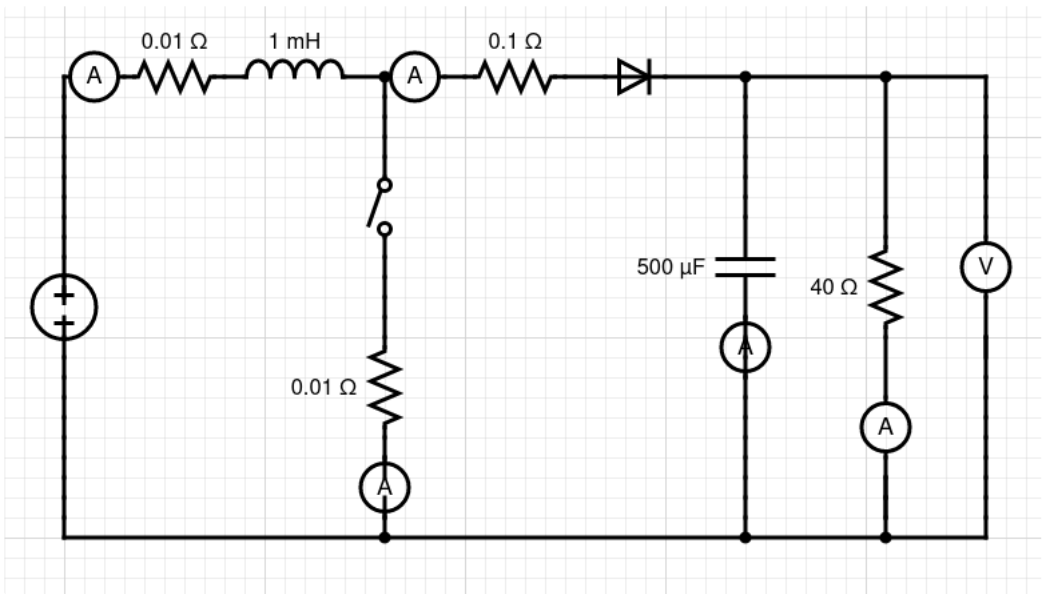
## Simulation of Buck and Boost Converter

- Used **Python Power Electronics**
- Gate Signal generated using Ramp Carrier Waveform
- Choose **Duty Ratio** as **0.7** to boost **12V** to **40V**




- Compared Currents voltages with  $C = 50, 500$  and  $5000$  microFarad and  $L=1, 10$  mH.
- **Openloop Control** to reduce initial **spike**, something like **Slow Start**.
- DCM to CCM transition observed in openloop control.

## Interactive Graphs using Models


- Interactive Graph showing Duty Cycle needed to maintain constant  $V_{out}$ .
- Shows transition between DCM and CCM mode of operation

Duty Cycle vs Load Current

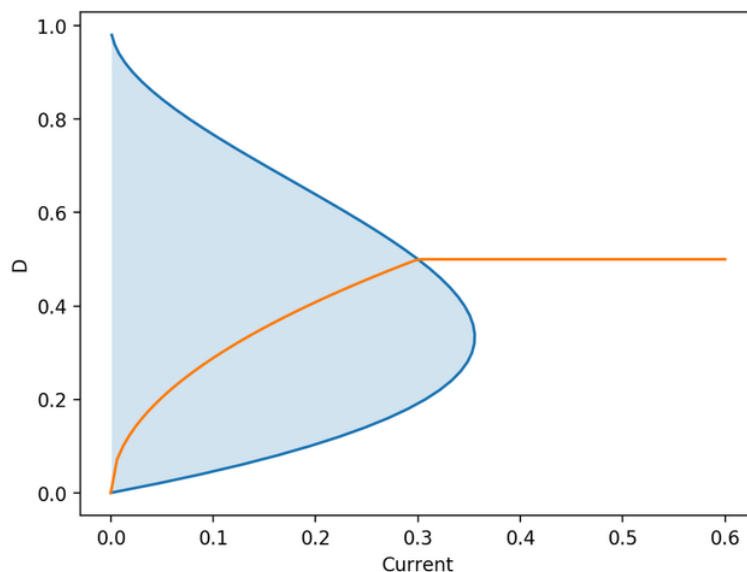

- Can't achieve infinite boost, because of inefficiencies.
- Used **small ripple approximation** to plot efficiency vs D and Boost vs D.
- Interactive graphs showing practical efficiency and boost
- Concatenating one boost after another to get better efficiency for same boost.

$\frac{V_{out}}{V_{in}}$  vs Duty Ratio

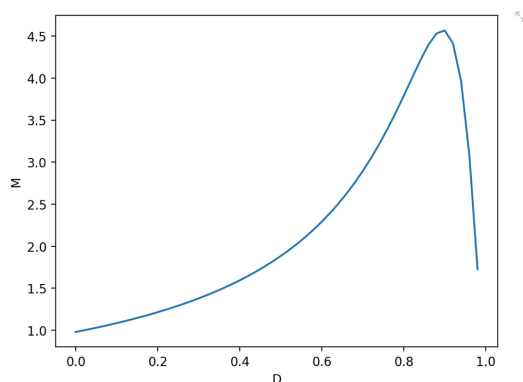

Efficiency vs Duty Ratio

